



University of California, Berkeley

# EE140 Operational Amplifier

# 1 Introduction

As the demand for mixed mode integrated circuits increases, the design of analog circuits such as operational amplifiers in CMOS technology becomes more critical. This technology has become an integral part of many integrated circuit chips fabricated today in a number of application areas. These amplifiers offer a number of advantages in terms of power dissipation, die area, and compatibility with digital circuits when compared to their bipolar counterparts.

In this paper we design and simulate a specific, widely used operational amplifier architecture, showing in detail how the formulation of the design variables takes place through a number of equations derived and calculated by hand. We then simulate the amplifier using HSPICE, presenting performance measures such as unity-gain bandwidth, open-loop gain, and settling time. We show how the proposed amplifier meets the specifications set in place by the project guidelines. We conclude with a discussion of the characteristics of the amplifier and the overall experience of the design project.

## 1.1 Circuit Schematic

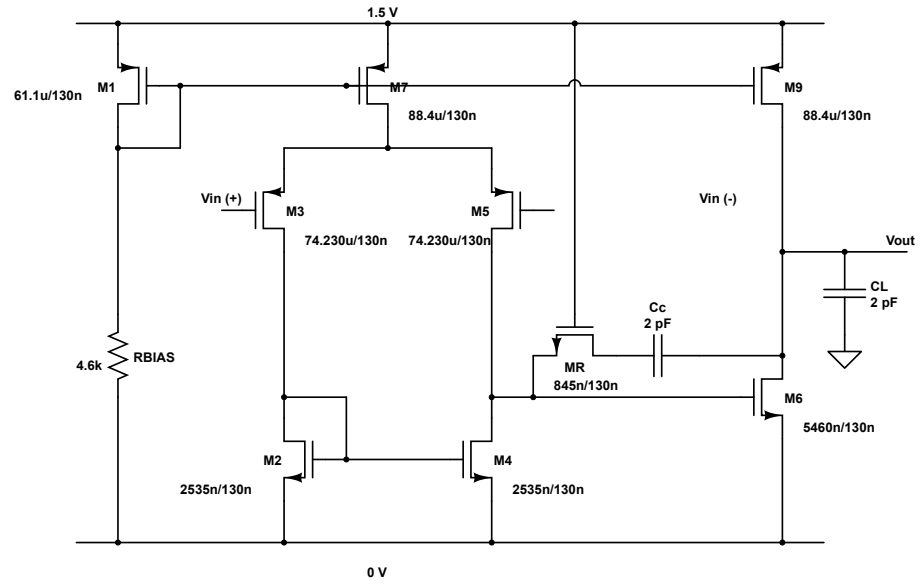


Figure 1: Two stage op-amp considered in this paper.

## 2 Part I: Hand Analysis

For the purposes of designing this amplifier, the design approach is as follows. First, we lay the groundwork for all important equations that must be considered in order to meet the specifications. We note dependencies and realize variables that enable design control. We then begin with the most rigorous specifications and choose our variables to be within margins that exceed the requirements, to provide a safety cushion against non-idealities. We keep all constraints in mind and finalize a design. We confirm that the requirements are met.

### 2.1 Equations

In this section, all of the relevant equations required to meet the specifications are listed for the purposes of demonstrating the interdependencies between variables and to illustrate the design process of the amplifier.

Specifications to be met:

- Gain  $\geq 1500$
- Output Swing : 1.2V
- Settling Time : 8ns with 0.4V step
- Unity Gain Frequency  $\geq 600MHz$
- Common Mode Input Range: 0.8V
- CMRR  $\geq 75dB$
- PSRR  $\geq 60dB|_{DC}$  50dB at 1MHz
- Power Dissipation: 1.5mW

### 2.1.1 Settling Time

To meet this specification, we will design our amplifier to have a slew rate that is one tenth of the settling time. Although this is not a one to one correspondence with the specification, settling time and slew rate are closely related, and achieving the above margin is a good indication that the spec has been met.<sup>1</sup>

$$SR = \frac{10V_0}{T_{s|0.1\%}}$$

$$T_{s|0.1\%} = 8ns \text{ with } 0.4V\text{Step}$$

$$SR = \frac{10(0.4)}{8ns}$$

$$SR = 500 \frac{V}{\mu S}$$

$$SR = \frac{I_{xm}}{C}$$

$$\boxed{\frac{I_{xm}}{C} \geq 5 \times 10^8 V/s}$$

where C is the largest capacitance in the circuit, and Ixm is the limiting current.

### 2.1.2 Unity Gain Frequency

$$ugf = \frac{gm_I}{C}$$

$$ugf = 2\pi 600MHz$$

$$\boxed{\frac{gm_I}{C} \geq 2\pi 600MHz}$$

### 2.1.3 Phase Margin

Phase margin, settling time, and unity gain frequency are all closely related and impact the stability of the circuit in feedback. Aiming for a target phase margin that is conducive to meeting the above two specs,

$$PM = 65^\circ$$

$$\omega_{p2} \geq \tan(65) \times 2\pi 600MHz$$

$$\boxed{\frac{gm_{II}}{C_I + C_{II}} \geq \tan(65) \times 2\pi 600MHz}$$

---

<sup>1</sup>C. T. Nguyen, Lecture 24, April 25, 2013

## 2.1.4 Gain

Total Gain:  $A_v = A_{v_1}A_{v_2}$

$$A_{v_1} = gm_3 \left( \frac{\frac{V_{A4}}{I_{D3}} \frac{V_{A5}}{I_{D3}}}{\frac{V_{A4}}{I_{D3}} + \frac{V_{A5}}{I_{D3}}} \right) \quad A_{v_2} = -gm_6 \left( \frac{\frac{V_{A6}}{I_{D6}} \frac{V_{A9}}{I_{D6}}}{\frac{V_{A6}}{I_{D6}} + \frac{V_{A9}}{I_{D6}}} \right)$$

$$A_v = \frac{-gm_3gm_6}{I_{D3}I_{D6}} \left( \frac{V_{A4}V_{A5}}{V_{A4} + V_{A5}} \right) \left( \frac{V_{A6}V_{A9}}{V_{A6} + V_{A9}} \right) \textcolor{red}{2}$$

Using the relation  $\frac{gm}{I_D} = \frac{2}{r_0}$  gives us

$$A_v = \frac{-4}{V_{ov3}V_{ov6}} \left( \frac{\frac{1}{\lambda_n} \frac{1}{\lambda_p}}{\frac{1}{\lambda_n} + \frac{1}{\lambda_p}} \right)^2$$

$$A_v = \frac{32.65}{V_{ov3}V_{ov6}}$$

$$\boxed{\frac{32.65}{V_{ov3}V_{ov6}} \geq 1500}$$

## 2.1.5 Output Swing

In order to satisfy an output swing of 1.2V we must satisfy the following:

$$V_{out,max} = V_{DD} - V_{ov9} = 1.35V$$

$$V_{out,min} = V_{ov6} = 0.15V$$

$$\boxed{V_{ov9} \leq 0.15V}$$

$$\boxed{V_{ov6} \leq 0.15V}$$

---

<sup>2</sup>Paul Gray, Robert Meyer, "Analysis and Design of Analog Integrated Circuits" (Wiley and Sons, 2010), 423

### 2.1.6 Common Mode Rejection Ratio

$$\text{CMRR} = \left| \frac{A_{dm}}{A_{cm}} \right|$$

The common mode rejection ratio is only dependent upon the first stage of the amplifier, because the second stage is a single ended input and output.

$$\begin{aligned} \text{CMRR} &= 2gm_3r_{07}gm_2(r_{03}||r_{02}) \\ &= \frac{4}{V_{ov3}V_{ov2}} \left( \frac{\frac{1}{\lambda_n} \frac{1}{\lambda_p}}{\frac{1}{\lambda_n} + \frac{1}{\lambda_p}} \right) \end{aligned} \quad \textcolor{red}{3}$$

$$\boxed{\frac{11.43}{V_{ov3}V_{ov2}} \geq 75dB}$$

### 2.1.7 Power Supply Rejection Ratio

In calculating the PSRR, we will neglect the variations due to the positive supply,  $V_{DD}$ . This is because  $PSRR_+ \rightarrow \infty$  for low frequencies with perfect matching<sup>4</sup>. This analysis is shown in G&M page 431.

Instead, we will calculate the PSRR that emerges due to variations from the  $V_{SS}$  supply, which in this case is ground.

$$A_- = \frac{v_o}{v_{ss}} = \frac{r_{09}}{r_{06} + r_{09}} = \frac{\frac{1}{\lambda_p}}{\frac{1}{\lambda_n} + \frac{1}{\lambda_p}} \quad \textcolor{red}{5}$$

$$PSRR = \frac{A_{dm}}{A_-}$$

$$\boxed{\frac{A_{dm}}{0.5714} \geq 60dB}$$

---

<sup>3</sup>Paul Gray, Robert Meyer, "Analysis and Design of Analog Integrated Circuits" (Wiley and Sons, 2010), 427

<sup>4</sup>Paul Gray, Robert Meyer, "Analysis and Design of Analog Integrated Circuits" (Wiley and Sons, 2010), 431

<sup>5</sup>Paul Gray, Robert Meyer, "Analysis and Design of Analog Integrated Circuits" (Wiley and Sons, 2010), 431

### 2.1.8 Common Mode Input Range

When  $V_{IC}$  is reduced to the point where  $V_{GD3} = V_{GD5} = V_{t3} = V_{t5}$ ,  $M3$  and  $M5$  operate at the edge of saturation. Thus, we define the lower end of the common mode input range to be :

$$V_{IC} \geq V_{t3} + V_{t2} + V_{ov2}$$

$$V_{IC} \geq V_{ov2}$$

The specification calls for a common mode input range that is  $0.8V$  inside the output swing range. This gives us a constraint on  $V_{ov2}$

$$V_{IC_{min}} = 0.15V$$

$$\boxed{V_{ov2} \leq 0.15V}$$

If  $V_{IC}$  is too high, we have  $M7$  falling into the triode region. Examining the drain voltage of  $M7$ ,

$$V_{DS7} = V_{IC} - V_{GS3} - V_{DD} = V_{IC} - V_{t3} - V_{ov3} - V_{DD}$$

Therefore,  $V_{IC}$  must satisfy the following:

$$V_{IC} < V_{DD} - |V_{t3}| - |V_{ov3}| - |V_{ov7}|$$

$$V_{IC} < 1.5 - 0.3 - |V_{ov3}| - 0.15$$

$$V_{IC} < 1.05 - |V_{ov3}|$$

From the specification,

$$V_{IC_{max}} = 0.95V$$

$$0.95 < 1.05 - |V_{ov3}|$$

$$\boxed{|V_{ov3}| < 0.100}$$



## 2.2 Design Equations and Sizing

In this section, we illustrate the design process of the amplifier. With the knowledge of the equations and constraints, we are able to make design decisions. These design decisions are based partly on intelligent speculations and in a large part on the equations and constraints. We complete the design with dimensions for each transistor and the value of the compensating capacitor,  $C_c$ .

For consistency with the load capacitance, we choose  $C_c$  to be 2pF. This gives us the following:

### 2.2.1 Slew Rate

$$\frac{I_{xm}}{2pF} \geq 500000000$$
$$I_{xm} \geq 1mA$$

### 2.2.2 Unity Gain Frequency

$$\frac{gm_I}{2pF} \geq 2\pi 600MHz$$
$$gm_I \geq 7.53mS$$

### 2.2.3 Output Swing

$$V_{ov9} \leq 0.15V$$

$$V_{ov6} \leq 0.15V$$

To have a comfortable margin, we set  $V_{ov6,9} = 0.09V$

### 2.2.4 Gain

$$\frac{32.65}{V_{ov3}V_{ov6}} \geq 1500$$

With  $V_{ov6} = 0.09$ ,

$$v_{ov3} \leq 0.24V$$

Set  $V_{ov3} = 0.1V$  to satisfy the common mode input range spec.

### 2.2.5 Sizing of M3, M5

To reduce capacitances and minimize power and current consumption, set all channel lengths to the minimum value,  $L_{min} = 130nm$ .

$$gm_3 = k'_p W/L(V_{ov})$$

$$0.00753 = k'_p W/L(0.1)$$

$$W/L_{3,5} = 73712/130$$

### 2.2.6 Sizing of M7, M9

As we can see from the settling time constraint, the circuit requires the maximum current we have available given the power restriction. With this in mind, we choose a reasonable value from experience and set the current through M9 to be 375 microamps and bias the output at half of the supply voltage. In addition, we match transistors 7 and 9 to ensure that the settling time specification is met, since both transistors supply current through large capacitors.

$$0.5k'_p(W/L)(V_{ov})^2(1 + 0.15(V_{SD})) = 375\mu A$$

$$0.5k'_p(W/L)(0.09)^2(1 + 0.15(0.75)) = 375\mu A$$

$$W/L_{7,9} = 81474/130$$

### 2.2.7 Sizing of M1

In order to meet the power dissipation requirement, the current through M1 must be no more than 250 microamps.

$$0.5k'_p(W/L)(V_{ov})^2(1 + 0.15(V_{ov} + V_t)) = 250\mu A$$

$$0.5k'_p(W/L)(0.09)^2(1 + 0.15(0.39)) = 250\mu A$$

$$W/L_1 = 57087/130$$

### 2.2.8 Sizing of M6

$$0.5k'_n(W/L)(V_{ov})^2(1 + 0.2(0.75)) = 375\mu A$$

$$0.5k'_n(W/L)(0.09)^2(1 + 0.2(0.75)) = 375\mu A$$

$$W/L_6 = 31527/130$$

### 2.2.9 Sizing of M2, M4

From common mode input range,

$$V_{ov2,4} \leq 0.15V$$

At equality we have,

$$0.5k'_n(W/L)(V_{ov})^2(1 + 0.2(V_{DS})) = 188\mu A$$

The drain-source voltage of M4 is the  $V_{gs}$  of M6. With this in mind,

$$0.5k'_n(W/L)(0.15)^2(1 + 0.2(0.39)) = 188\mu A$$

$$W/L_{2,4} = 6053/130$$

### 2.2.10 RHP Zero

We want to set the resistor,  $R_z$ , to a value such that the zero introduced by the circuit is pushed out to infinity. To do this we set,

$$R_z = 1/gm_{II}$$

$$gm_{II} = k'_n W/L(V_{ov}) = 7.24mS$$

$$R_z = 138\Omega$$

$$R_z = L/(Wk'_n(V_{GS} - V_t))$$

$$W/L_r = 2012/130$$

### 2.2.11 Frequency Response

We would like to impart a phase margin of 60 degrees or better to offer a circuit that is stable under unity gain feedback and yields a quick settling time for sharp rising signals. To this end, we must push the second pole out past the value shown in the equations section above. In order to satisfy this, we must meet the following constraint,

$$C_I + C_{II} \leq 8.96 \times 10^{-13}$$

The calculations involving the derivation of the capacitances is shown in a MATLAB script below and we can see that the requirement is met. We have included the estimated areas and relevant perimeters of the drain and source of the transistors as per the project guidelines.

## Contents

- [Derivation of all parameter values](#)
- [Determination of all parasitics](#)
- [Equations](#)
- [Final Result](#)

```
% Frequency Response MATLAB Script
```

## Derivation of all parameter values

```
mu_n = 0.025; % units: m^2/(Vs)
mu_p = 0.010; % units: m^2/(Vs)

e_ox = 3.9*8.854E-12; % units: F/m
t_ox = 2.6E-9; % units: m

c_ox = e_ox/t_ox; % units: F/m^2

k_n = mu_n*c_ox; % units: A/V^2
k_p = mu_p*c_ox; % units: A/V^2
```

## Determination of all parasitics

```
% relevant parasitic capacitances: cgd4, cdb4, cgd5, cdb5, cgs6, cgd6,
% cdb6, cgd9, cdb9, cdb_r, cgs_r, csb_r, cgd_r
syms W4 L4 W5 L5 W6 L6 W9 L9 W_r L_r vdb4 vdb5 vdb6 vdb9 av_II

% Device Dimensions

W3 = 73712E-9;
L3 = 130E-9;
W5 = 73712E-9;
L5 = 130E-9;
W9 = 81474E-9;
L9 = 130E-9;
W6 = 31527E-9;
L6 = 130E-9;
vdb4 = 0.12;
vdb5 = 0.12;
vdb6 = 0.75;
vdb9 = 0.75;
gm_II = 7.24E-3;
ro_6 = 1/(0.2*376E-6);
ro_9 = 1/(0.15*376E-6);
rout = (1/ro_6+1/ro_9)^(-1);
av_II = gm_II*rout;
W_r=2012E-9;
L_r=130E-9;
W4=6053E-9;
L4 =130E-9;
```

### % Device Capacitances

```
c_j = 8E-4; % units: F/m^2
c_jsw = 8E-10; % units: F/m
LD = 2.5E-8; % units: m
```

### % gate-drain

```
cgd4 = W4*LD*c_ox; % units: F
cgd5 = W5*LD*c_ox; % units: F
cgd6 = W6*LD*c_ox; % units: F
cgd9 = W9*LD*c_ox; % units: F
cgd_r = W_r*LD*c_ox; % units: F
```

### % gate-source

```
cgs6 = (2/3)*W6*L6*c_ox + cgd6; % units: F
cgs_r = (2/3)*W_r*L_r*c_ox + cgd_r; % units: F
```

### % drain-body & source-body

```
lambda_4 = L4/2; % units: m
lambda_5 = L5/2; % units: m
lambda_6 = L6/2; % units: m
lambda_9 = L9/2; % units: m
lambda_r = L_r/2; % units: m
```

```
cdb4 = ( W4*(5*lambda_4)*c_j + (W4 + 2*(5*lambda_4))*c_jsw ) / sqrt(1+vdb4/0.8); % u
cdb5 = ( W5*(5*lambda_5)*c_j + (W5 + 2*(5*lambda_5))*c_jsw ) / sqrt(1+vdb5/0.8); % u
cdb6 = ( W6*(5*lambda_6)*c_j + (W6 + 2*(5*lambda_6))*c_jsw ) / sqrt(1+vdb6/0.8); % u
cdb9 = ( W9*(5*lambda_9)*c_j + (W9 + 2*(5*lambda_9))*c_jsw ) / sqrt(1+vdb9/0.8); % u
csb_r = ( W_r*(5*lambda_r)*c_j + (W_r + 2*(5*lambda_r))*c_jsw ); % units: F
```

## Equations

```
C_I = cdb5 + cdb4 + cgd4 + cgd5 + cgs_r + cgs6 + csb_r + cgd6*(1+av_II);
C_II = cdb6 + cdb9 + cgd9 + cgd6 + cgd_r;
```

### % Approximations:

```
% C_I = cgd4 + cgd5+ cgs6 + (1+av_II)*cgd6;
% C_II = cgd6 + cgd9;
```

## Final Result

```
C_I_plus_C_II = C_I + C_II
```

```
C_I_plus_C_II =
```

```
8.7003e-13
```

### 3 Part II: Simulation

We go from the design parameters we have just derived and simulate the op-amp in hspice. We make adjustments to certain dimensions as necessary for biasing. For instance, the width of M6 had to be reduced in order to allow for saturation conditions for all transistors. Other transistors were adjusted to reduce power consumption. We make adjustments to certain dimensions as necessary for the fulfillment of specifications as well. Slight tweaking of all transistors is required in order to comply with the 65nm technology used for this design. Transistors were also sized to reduce or increase overdrive voltages. Through many iterations, the devices are sized in such a way that the project parameters are all met. Dimensions used in the simulation of the circuit are within 10 percent of the estimated values except where noted. Wherever variances lie, the hand calculated values rectify these disparities when the values in the equations used in the above calculations are substituted with values from the simulation.

We have met all of the specifications called for in the design and have done so adequately. Graphs, tables and simulated values are now shown to substantiate the performance of this op-amp.

## 3.1 Transistor and Bias Summary

### 3.1.1 Biasing and small signal parameters

As we can see, all bias currents are within 10% of hand calculated values. The overdrive voltage of  $M1, 7, 9$  were further reduced to increase efficiency.

```
Using: /bin/time /share/instsw/synopsys/C-2009.09/hspice/sparc055/hspice CMOS.sp
***** HSPICE -- C-2009.09 32-BIT (Aug 24 2009) sunos *****
Copyright (C) 2009 Synopsys, Inc. All Rights Reserved.
Unpublished-rights reserved under US copyright laws.
This program is protected by law and is subject to the
terms and conditions of the license agreement from Synopsys.
Use of this program is your acceptance to be bound by the
license agreement. HSPICE is the trademark of Synopsys, Inc.
Input File: CMOS.sp
lic:
lic: FLEXlm: v8.5b
lic: USER: ee140-cw          HOSTNAME: quasar
lic: HOSTID: 83846a81        PID: 16944
lic: Using FLEXlm license file:
lic: 27005@license-srv.eecs.berkeley.edu
lic: Checkout 1 hspice
lic: License/Maintenance for hspice will expire on 25-oct-2013/2012.06
lic: FLOATING license(s) on SERVER license-srv.eecs.berkeley.edu
lic:
Init: read install configuration file: /share/instsw/synopsys/C-2009.09/hspice/meta.cfg
1***** HSPICE -- C-2009.09 32-BIT (Aug 24 2009) sunos *****
*****
** ee140 lab3 : cmos operational amplifier design **

***** circuit name directory
circuit number to circuit name directory
number circuitname          definition          multiplier
  0 main circuit
  1 x7.                      pmos          1.00
  2 x3.                      pmos          1.00
  3 x5.                      pmos          1.00
  4 x2.                      nmos          1.00
  5 x4.                      nmos          1.00
  6 x6.                      nmos          1.00
  7 x9.                      pmos          1.00
  8 xr.                      nmos          1.00
  9 x1.                      pmos          1.00
**warning** (model_ee140_1.sp:14) both nodes of element x2.csbnn defined in subckt nmos are connected together.

**diagnostic** set option symb=1 internally to help for convergence.
***** option summary
*****
runlvl = 3          bypass = 2
opening plot unit= 15
file=CMOS.pa0

1***** HSPICE -- C-2009.09 32-BIT (Aug 24 2009) sunos *****
*****
** ee140 lab3 : cmos operational amplifier design **

***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node      =voltage      node      =voltage      node      =voltage
+0:cm      = 750.0000m 0:drain_m2= 484.7740m 0:gate_m3 = 750.0000m
+0:gate_m5 = 750.0000m 0:node      = 484.7740m 0:out_1  = 484.7740m
+0:out_2   = 575.1228m 0:tail     = 1.1440  0:vbias   = 1.1283
+0:vdd     = 1.5000

**** voltage sources
subckt
element 0:v1      0:vcm      0:vid1      0:vid2
volts   1.5000    750.0000m 0.         0.
current -988.2479u 0.         0.         0.
power   1.4824m    0.         0.         0.

total voltage source power dissipation= 1.4824m watts

**** resistors
subckt
element 0:rbias
r value 4.6000k
v drop 1.1283
current 245.2751u
power 276.7353u
```

```

**** mosfets

subckt x7 x3 x5 x2 x4 x6
element 1:m0 2:m0 3:m0 4:m0 5:m0 6:m0
model 1:pmos_int 2:pmos_int 3:pmos_int 4:nmos_int 5:nmos_int 6:nmos_int
region Saturati Saturati Saturati Saturati Saturati Saturati
id -353.9799u -176.9900u -176.9900u 176.9900u 176.9900u 388.9928u
ibs 0. 3.5598f 3.5598f 0. 0. 0.
ibd 3.5598f 10.1523f 10.1523f -4.8477f -4.8477f -5.7512f
vgs -371.7348m -394.0227m -394.0227m 484.7740m 484.7740m 484.7740m
vds -355.9773m -659.2488m -659.2488m 484.7740m 484.7740m 575.1228m
vbs 0. 355.9773m 355.9773m 0. 0. 0.
vth -300.0000m -340.6288m -340.6288m 300.0000m 300.0000m 300.0000m
vdsat -63.7165m -48.4953m -48.4953m 164.7889m 164.7889m 164.7889m
vod -71.7348m -53.3939m -53.3939m 184.7740m 184.7740m 184.7740m
beta 155.0371m 136.7577m 136.7577m 11.6509m 11.6509m 25.6066m
gam_eff 200.0000m 200.0000m 200.0000m 200.0000m 200.0000m 200.0000m
gm 9.8784m 6.6321m 6.6321m 1.9199m 1.9199m 4.2197m
gds 56.0921u 29.4619u 29.4619u 39.1985u 39.1985u 87.9104u
gmb 1.2431m 669.9182u 669.9182u 232.8444u 232.8444u 511.7510u
cdtot 51.5411f 39.8846f 39.8846f 1.4521f 1.4521f 3.0044f
cgtot 121.3208f 101.8738f 101.8738f 3.4791f 3.4791f 7.4933f
cstot 118.1396f 95.8601f 95.8601f 3.3919f 3.3919f 7.3008f
cbtot 48.3599f 33.8709f 33.8709f 1.3649f 1.3649f 2.8919f
cgs 91.9690f 77.2269f 77.2269f 2.6373f 2.6373f 5.6804f
cgd 29.3517f 24.6468f 24.6468f 841.7038a 841.7038a 1.8129f

subckt x9 xr x1
element 7:m0 8:m0 9:m0
model 7:pmos_int 8:nmos_int 9:pmos_int
region Saturati Linear Saturati
id -388.9928u 0. -245.2751u
ibs 0. 0. 0.
ibd 9.2488f 8.455e-25 3.7173f
vgs -371.7348m 1.0152 -371.7348m
vds -924.8772m -2.1722p -371.7348m
vbs 0. 0. 0.
vth -300.0000m 300.0000m -300.0000m
vdsat -63.7165m 646.8229m -63.7165m
vod -71.7348m 715.2260m -71.7348m
beta 170.3721m 3.5071m 107.4262m
gam_eff 200.0000m 200.0000m 200.0000m
gm 10.8555m 0. 6.8448m
gds 66.0905u 2.5084m 38.9639u
gmb 1.3661m 0. 861.3714u
cdtot 47.9142f 983.7589a 35.5326f
cgtot 121.3208f 1.4590f 83.8541f
cstot 118.1396f 983.7589a 81.6566f
cbtot 44.7331f 508.5600a 33.3351f
cgs 91.9690f 729.4789a 63.5668f
cgd 29.3517f 729.4789a 20.2872f

***** job concluded
1***** HSPICE -- C-2009.09 32-BIT (Aug 24 2009) sunos *****
*****
** ee140 lab3 : cmos operational amplifier design **

***** job statistics summary tnom= 25.000 temp= 25.000 *****

***** HSPICE Threads Information *****

Command Line Threads Count : 1
Available CPU Count : 4
Actual Model Evaluation(Load) Threads Count : 1
Actual Solver Threads Count : 1

***** Circuit Statistics *****
# nodes = 11 # elements = 22
# resistors = 1 # capacitors = 8 # inductors = 0
# mutual_inds = 0 # vcvs = 0 # vcvcs = 0
# cccs = 0 # ccvs = 0 # volt_srcs = 4
# curr_srcs = 0 # diodes = 0 # bjts = 0
# jfets = 0 # mosfets = 9 # U elements = 0
# T elements = 0 # W elements = 0 # B elements = 0

```

Figure 2: Summary of biasing and small signal parameters simulated in hspice



### 3.1.2 Transistor Dimensions

All transistor sizes are within 10% of the expected values from the hand calculations with the exception of  $M2, 4, 6$  and  $MR$ .  $M6$  was manually resized to secure saturation conditions across all transistors. The simulation shows that this transistor is in the linear region when the size is in the range of the hand calculated value. The size of  $M6$  was reduced until the transistor was saturated and the output voltage was biased at a value close to  $0.75V$ . A similar procedure was initially taken with  $M2, 4$ .  $MR$  was manually resized to provide a good phase margin. We are able to manually resize this device by pulling the newly simulated value of  $gm_{II}$  and adjusting the width until the resistance is approximately equal to  $1/gm_{II}$ . The result is a circuit that matches all other expected values to within 10% or better.

Transistor	Width	Length	————
M1	61,100nm	130nm	
M2	2,535nm	130nm	
M4	2,535nm	130nm	
M3	74,230nm	130nm	
M5	74,230nm	130nm	
M6	5,460nm	130nm	
M7	88,400nm	130nm	
M9	88,400nm	130nm	
MR	845nm	130nm	

Figure 3: Table of device dimensions.

### 3.2 Performance Summary

Parameter	Specification	Circuit Performance	Spec Met?
DC Gain	1500	5121	Yes
Common Mode Input Range	0.8V	1.35V	Yes
Output Swing	1.2V	1.275V	Yes
Power Dissipation	1.5mW	1.48mW	Yes
Unity Gain Frequency	600 MHz	725 MHz	Yes
Settling Time	8ns	7.8ns rising, 7.78ns falling	Yes
CMRR	75dB	83.2dB	Yes
PSRR at DC	60dB	92dB	Yes
PSRR at 1MHz	50dB	94.7dB	Yes
Lmin	130nm	130nm	Yes
Wmin	195nm	845nm	Yes
Temperature	25C	25C	Yes

Figure 4: Table of simulated specifications

### 3.3 DC Gain, Phase Margin, and Unity Gain Frequency

The graphs below show the simulated results of the amplifier's open loop gain, frequency response, and phase margin at unity gain.

#### 3.3.1 DC Gain

 


Figure 5: The differential gain of the amplifier is  $74.18dB$

...

### 3.3.2 Unity Gain Frequency

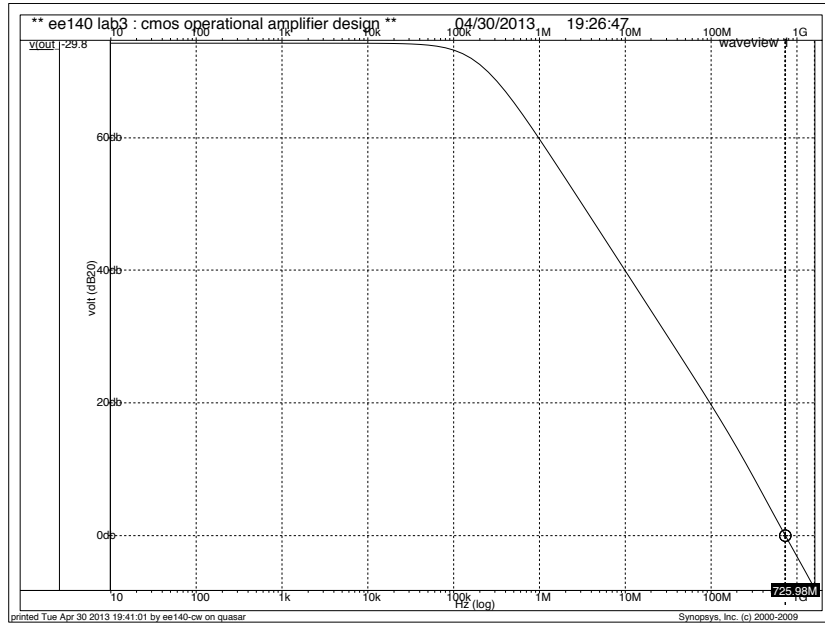


Figure 6: The unity gain frequency of the amplifier is  $725.98\text{MHz}$

### 3.3.3 Phase

 


Figure 7: The phase at unity gain is  $-113^\circ$ . The phase margin at unity is  $67^\circ$

### 3.4 CMRR and PSRR

The graph below shows the amplifier's common mode rejection ratio and power supply rejection ratio. By taking the ratio of the common mode gain to the differential mode gain, we compute the common mode rejection ratio. By taking the ratio of the power supply gain to the differential mode gain, we compute the power supply rejection ratio. These values can be found in figure 3 above.

Note that the power supply gain from the negative source can be computed by the equation offered in section 2.1.7. With the amplifier providing a gain on the order of 74dB at low frequencies and roughly 60dB at 1MHz, it is clear that  $PSRR_- > 60dB$ .

#### 3.4.1 Common mode gain

 


Figure 8: The common mode gain of the amplifier is  $-9.03dB$

### 3.4.2 Power supply gain at DC

 


Figure 9: The power supply gain at  $DC$  is  $-17.9dB$

### 3.4.3 Power supply gain at 1MHz

 


Figure 10: The power supply gain at  $1MHz$  is  $-20.5dB$

### 3.5 Common Mode Input Range

This is defined as the range of voltages at which  $dV_{out}/dV_{in}$  becomes 1/2 in unity gain feedback. To show this, we put the op amp into unity gain configuration and sweep the  $DC$  voltage at the input from 0 to  $V_{DD}$ . The graphs below show the maximum and minimum of this range. This amplifier exceeds the specification by a relatively large margin. This is partly due to tying the bulk to  $V_{DD}$  in  $M3,5$ . This was done because the body effect on the input transistors can be used to increase the range<sup>6</sup>. The total common mode input range of the amplifier is listed in figure 3.

#### 3.5.1 Common Mode Input Range, minimum

 


Figure 11: The minimum value corresponds to an output voltage of 0.115V

#### 3.5.2 Common Mode Input Range, maximum

 


Figure 12: The maximum value corresponds to an output voltage of 1.47V

### 3.6 Output Swing

This is defined as the range of voltages at which  $dV_{out}/dV_{in}$  becomes  $1/10^{th}$  the nominal differential gain. To show this, we sweep the  $DC$  voltage at one of the inputs around its bias points and find the points on the curve where the derivative is approximately equal to  $1/10^{th}$  of the nominal gain. The graphs below show the minimum and maximum of this range. The total output swing of the amplifier is listed in figure 3.

#### 3.6.1 Output Swing, minimum

 


Figure 13: The minimum value corresponds to an output voltage of 0.168V

#### 3.6.2 Output Swing, maximum

 


Figure 14: The maximum value corresponds to an output voltage of 1.44V



### 3.7 Settling Time

This is the most stringent specification to meet, as it requires relatively large amounts of current to be supplied from the current sources. We measure settling time by putting the op amp into unity gain feedback and applying a  $0.4V$  step to the input. We then run a transient analysis in hspice to determine the time it takes for the amplifier's output to converge to within 0.1%. The time it takes to converge must be under 8ns.

In order to meet this specification, some changes to device dimensions were made in order to increase the current to a value high enough to just meet the spec. Increasing the sizes of the current sources allowed for a better settling time; the drawback however, is that power consumption became excessive. To ameliorate this, the size of the biasing transistor was reduced and the bias resistor increased in order to preserve roughly the same overdrive voltage. The result is an amplifier that has a settling time of just under 8ns and consumes less than  $1.5mW$  of power.

#### 3.7.1 Settling Time

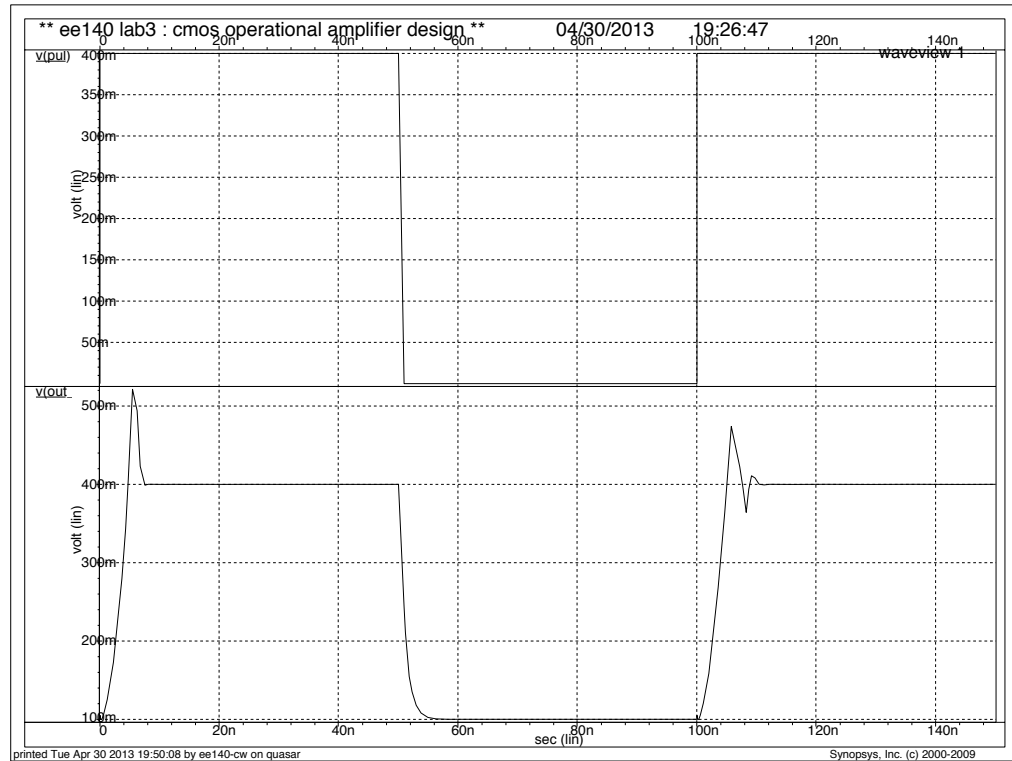


Figure 15:  $0.4V$  step input and amplifier response

### 3.7.2 Settling Time, rising input

 


Figure 16: The time it takes to converge on a rising input is  $7.88ns$

### 3.7.3 Settling Time, falling input

 


Figure 17: The time it takes to converge on a falling input is  $7.78ns$

## 4 Conclusion

We have shown the design process of an analog integrated circuit CMOS operational amplifier, and we have shown how equations we have derived throughout the semester participate in this process. We have seen how tradeoffs must be made between certain parameters in order to provide an amplifier that is balanced and meets a wide range of specifications. For the most part, the amplifier considered in this paper is ideal for use in digital circuits or mixed signal circuits where the characteristics of the stages connected to the op-amp are known in advance. This amplifier provides a good gain for digital signals (digital signals typically do not require as much gain as their analog counterparts), a wide bandwidth, stellar phase margin for gains down to and below unity, a very quick settling time, and consumes very little power. Furthermore, the amplifier has a very good power supply rejection ratio which offers outstanding performance in digital circuits with high levels of switching noise. Overall, the amplifier we have designed is a stable, low power op-amp that is the quintessential CMOS operational amplifier utilized by engineers throughout the world.

The design of this op amp was a scrupulous and testing process, and a tremendous learning experience as well. To see how all of the many variables depended on each other required me to think in a way that I have never before and forced me to stretch myself; to think in ways I had never thought in previously. Arguably, a better way to design a circuit like this is to write a geometric program and have a computer automatically compute a robust design given the parameters and specifications. This implies that the circuit designer can spend more time doing real design, *i.e.*, carefully analyzing the optimal trade-offs between competing objectives and less time doing parameter tuning or wondering whether a certain set of specifications can be achieved. However, for the purposes of this course and the learning experience required to become a competent circuit designer, it is necessary to do this type of analysis by hand and think about the circuit ourselves, rather than have a computer do the thinking for us. At the end of the day, I can say that I have a solid grasp and comprehension of the way a relatively large MOS circuit like this operates. I realize the interdependencies between variables like dimension, transconductance, and overdrive voltage, and I acknowledge the tradeoffs required to satisfactorily meet an extensive range of specifications. Overall, the wisdom and erudition bestowed upon me as a result of successfully completing this project is immense, and it was undeniably worth the effort.